

Delmar's Standard Textbook of Electricity

Third Edition

Table of Contents

Section 1 - Safety, Electricity and Ohm's Law	2
--	----------

Safety Overview

S-1 General Safety Rules	4
S-2 Effects of Electric Current on the Body	6
S-3 On the Job	7
S-4 Protective Clothing	12
S-5 Ladders and Scaffolds	16
S-6 Fires	18
S-7 Ground-Fault Circuit Interrupters	20
S-8 Grounding	22

Unit 1 - Atomic Structure	28
--	-----------

1-1 Early History of Electricity	29
1-2 Atoms	31
1-3 The Law of Charges	34
1-4 Centripetal Force	36
1-5 Electron Orbits	37
1-6 Valence Electrons	39
1-7 Electron Flow	40
1-8 Insulators	43
1-9 Semiconductors	44
1-10 Molecules	44
1-11 Methods of Producing Electricity	46
1-12 Electrical Effects	47

Unit 2 - Electrical Quantities and Ohm's Law	51
---	-----------

2-1 The Coulomb	52
2-2 The Ampere	53
2-3 The Electron Flow Theory	54

2-4 The Conventional Current Flow Theory	54
2-5 Speed of Current	56
2-6 Basic Electric Circuits	59
2-7 The Volt	61
2-8 The Ohm	62
2-9 The Watt	64
2-10 Other Measures of Power	66
2-11 Ohm's Law	68
2-12 Metric Prefixes	73
Unit 3 - Static Electricity	79
3-1 Static Electricity	80
3-2 Charging an Object	82
3-3 The Electroscope	82
3-4 Static Electricity in Nature	85
3-5 Nuisance Static Charges	88
3-6 Useful Static Charges	89
Unit 4 - Magnetism	94
4-1 The Earth Is a Magnet	95
4-2 Permanent Magnets	97
4-3 The Electron Theory of Magnetism	97
4-4 Magnetic Materials	99
4-5 Magnetic Lines of Force	100
4-6 Electromagnets	101
4-7 Magnetic Measurement	105
4-8 Magnetic Polarity	107
4-9 Demagnetizing	107
4-10 Magnetic Devices	109
Unit 5 - Resistors	112
5-1 Uses of Resistors	113
5-2 Fixed Resistors	114
5-3 Color Code	118

5-4 Standard Resistance Values of Fixed Resistors	124
5-5 Power Ratings	126
5-6 Variable Resistors	127
5-7 Schematic Symbols	130
Section 2 - Basic Electric Circuits	134
Unit 6 - Series Circuits	135
6-1 Series Circuits	136
6-2 Voltage Drops in a Series Circuit	137
6-3 Resistance in a Series Circuit	139
6-4 Calculating Series Circuit Values	139
6-5 Solving Circuits	141
6-6 Voltage Dividers	154
6-7 The General Voltage Divider Formula	156
6-8 Voltage Polarity	157
6-9 Using Ground as a reference	158
Unit 7 - Parallel Circuits	162
7-1 Parallel Circuit Values	163
7-2 Parallel Resistance Formulas	166
Unit 8 - Combination Circuits	188
8-1 Combination Circuits	189
8-2 Solving Combination Circuits	190
8-3 Simplifying the Circuit	191
8-4 Other Electrical Laws	209
Section 3 - Meters and Wire Sizes	244
Unit 9 - Measuring Instruments	245
9-1 Analog Meters	246
9-2 The Voltmeter	251
9-3 Multirange Voltmeters	252

9-4 Reading a Meter	255
9-5 The Ammeter	258
9-6 Ammeter Shunts	259
9-7 Multirange Ammeters	262
9-8 The Ayrton Shunt	262
9-9 AC Ammeters	267
9-10 Clamp-on Meters	271
9-11 DC-AC Clamp-on Ammeters	274
9-12 The Ohmmeter	277
9-13 Shunt-type Ohmmeters	279
9-14 Digital Meters	280
9-15 The Low-Impedance Voltage Tester	283
9-16 The Oscilloscope	285
9-17 The Wattmeter	296
9-18 Recording Meters	298
9-19 Bridge Circuits	298
Unit 10 - Using Wire Tables and Determining Conductor Sizes	305
10-1 Using the NEC® Charts	306
10-2 Factors that Determine Ampacity	311
10-3 Correction Factors	312
10-4 Computing conductor Sizes and resistance	316
10-5 Computing Voltage Drop	327
10-6 Parallel Conductors	328
10-7 Testing Wire Installations	331
Section 4 - Small Sources of Electricity	338
Unit 11 - Conduction in Liquids and Gases	339
11-1 The Ionization Process: Magnesium and Chlorine	340
11-2 Other Types of Ions	342
11-3 Electroplating	344
11-4 Electrolysis	345
11-5 Conduction in Gases	345

11-6 Ionization in Nature	350
Unit 12 - Batteries and Other Sources of Electricity	353
12-1 History of the Battery	354
12-2 Cells	356
12-3 Cell Voltage	357
12-4 Primary Cells	359
12-5 Secondary Cells: Lead-Acid Batteries	367
12-6 Other Secondary Cells	374
12-7 Series and Parallel Battery Connections	377
12-8 Other Small Sources of Electricity	379
Unit 13 - Magnetic Induction	388
13-1 Electromagnetic Induction	389
13-2 Fleming's Left-Hand Generator Rule	392
13-3 Moving Magnetic Fields	393
13-4 Determining the Amount of Induced Voltage	393
13-5 Lenz's Law	394
13-6 Rising Time of Current in an Inductor	397
13-7 The Exponential Curve	399
13-8 Inductance	401
13-9 R-L Time Constants	403
13-10 Induced Voltage Spikes	404
Section 5 - Basics of Alternating Current (AC)	412
Unit 14 - Basic Trigonometry and Vectors	413
14-1 Right Triangles	414
14-2 The Pythagorean Theorem	415
14-3 Sines, Cosines and Tangents	417
14-4 Formulas	421
14-5 Practical Application	421
Unit 15 - Alternating Current (AC)	434

15-1 Advantages of AC	435
15-2 AC Waveforms	436
15-3 Sine Wave Values	442
15-4 Resistive Loads	450
15-5 Power in an AC Circuit	451
15-6 Skin Effect in AC Circuits	452
Section 6 - Alternating Current Circuits Containing Inductance	458
Unit 16 - Inductance in AC Circuits	459
16-1 Inductance	460
16-2 Inductive Reactance	463
16-3 Schematic Symbols	467
16-4 Inductors Connected in Series	468
16-5 Inductors Connected in Parallel	469
16-6 Voltage and Current Relationships in an Inductive Circuit	471
16-7 Power in an Inductive Circuit	473
16-8 Reactive Power	474
16-9 Q of an Inductor	474
Unit 17 - Resistive-Inductive Series Circuits	480
17-1 R-L Series circuits	481
17-2 Impedance	483
17-3 Total Current	485
17-4 Voltage Drop across the Resistor	486
17-5 Watts	487
17-6 Computing the Inductance	488
17-7 Voltage Drop across the Inductor	488
17-8 Total Voltage	489
17-9 Computing the Reactive Power	490
17-10 Computing the Apparent Power	491
17-11 Power Factor	493
17-12 Angle Theta	494

Unit 18 - Resistive-Inductive Parallel Circuits	508
18-1 Resistive-Inductive Parallel Circuits	509
18-2 Computing Circuit Values	510
 Section 7 - AC Circuits Containing Capacitors	 528
 Unit 19 - Capacitor	 529
19-1 Capacitors	530
19-2 Electrostatic Charge	533
19-3 Dielectric Constants	537
19-4 Capacitor Ratings	538
19-5 Capacitors Connected in Parallel	539
19-6 Capacitors Connected in Series	540
19-7 Capacitive Charge and Discharge Rates	541
19-8 RC Time Constants	543
19-9 Applications for Capacitors	545
19-10 Nonpolarized Capacitors	545
19-11 Polarized Capacitors	548
19-12 Variable Capacitors	551
19-13 Capacitor Markings	553
19-14 Temperature Coefficients	555
19-15 Ceramic Capacitors	555
19-16 Dipped Tantalum Capacitors	556
19-17 Film Capacitors	556
19-18 Testing Capacitors	557
 Unit 20 - Resistive-Capacitive Series Circuits	 563
20-1 Connecting the Capacitor into an AC Circuit	564
20-2 Capacitive Reactance	566
20-3 Computing Capacitance	567
20-4 Voltage & Current Relationships in a Pure Capacitive Circuit.	568
20-5 Power in a Pure Capacitive Circuit	570
20-6 Quality of a Capacitor	571
20-7 Capacitor Voltage Ratings	572

20-8 Effects of Frequency in a Capacitive Circuit573

20-9 Series Capacitors574

20-10 Parallel Capacitors579

Unit 21 - Resistive-Capacitive Series Circuits585

21-1 Resistive-Capacitive Series Circuits586

21-2 Impedance587

21-3 Total Current588

21-4 Voltage Drop across the Resistor589

21-5 True Power589

21-6 Capacitance589

21-7 Voltage Drop across the Capacitor590

21-8 Total Voltage590

21-9 Reactive Power591

21-10 Apparent Power591

21-11 Power Factor592

21-12 Angle Theta592

Unit 22 - Resistive-Capacitive Parallel Circuits602

22-1 Operation of RC Parallel Circuits603

22-2 Computing Circuit Values604

**Section 8 - AC Circuits Containing Resistance-Inductance-
Capacitance618**

Unit 23 - Resistive-Inductive-Capacitive Series Circuits619

23-1 RLC Series Circuits620

23-2 Series Resonant Circuits631

Unit 24 - Resistive-Inductive-Capacitive Parallel Circuits640

24-1 RLC Parallel Circuits641

24-2 Parallel Resonant Circuits650

Unit 25 - Filters	664
25-1 Broad-Band Tuning	666
25-2 Low-Pass Filters	667
25-3 High-Pass Filters	669
25-4 Bandpass Filters	672
25-5 Band-Rejection (Notch) Filters	673
25-6 T Filters	675
25-7 PI-Type Filters	676
25-8 Crossover Networks	676
Section 9 - Three-Phase Power	680
Unit 26 - Three-Phase Circuits	681
26-1 Three-Phase Circuits	682
26-2 Wye Connections	684
26-3 Delta Connections	688
26-4 Three-Phase Power	689
26-5 Watts and VARS	690
26-6 Three-Phase Circuit Calculations	691
26-7 Load 3 Calculations	700
26-8 Load 2 Calculations	700
26-9 Load 1 Calculations	701
26-10 Alternator Calculations	702
26-11 Power Factor Correction	703
Section 10 - Transformers	710
Unit 27 - Single-Phase Transformers	711
27-1 Single-Phase Transformers	712
27-2 Isolation Transformers	714
27-3 Autotransformers	740
27-4 Transformer Polarities	743
27-5 Voltage and Current Relationships in a Transformer	748
27-6 Testing the Transformer	750

27-7 Transformer Nameplates	751
27-8 Determining Maximum Current	752
27-9 Transformer Impedance	753
Unit 28 - Three-Phase Transformers	760
28-1 Three-Phase Transformers	761
28-2 Closing a Delta	766
28-3 Three-Phase Transformer Calculations	767
28-4 Open-Delta Connection	773
28-5 Single-Phase Loads	774
28-6 Closed Delta with Center Tap	778
28-7 Closed Delta without Center Tap	779
28-8 Delta-Wye Connection with Neutral	780
28-9 T-Connected Transformers	781
28-10 Scott Connection	784
28-11 Zig-Zag Connection	784
28-12 Harmonics	786
Section 11- DC Machines	802
Unit 29 - DC Generators	803
29-1 What is a generator?	804
29-2 Armature Windings	814
29-3 Brushes	816
29-4 Pole Pieces	816
29-5 Field Windings	817
29-6 Series Generators	818
29-7 Shunt Generators	822
29-8 Compound Generators	828
29-9 Compounding	829
29-10 Countertorque	832
29-11 Armature Reaction	833
29-12 Setting the Neutral Plane	836
29-13 Paralleling Generators	837

Unit 30 - DC Motors	843
30-1 DC Motor Principles	844
30-2 Shunt Motors	847
30-3 Series Motors	850
30-4 Compound Motors	852
30-5 Terminal Identification for DC Motors	854
30-6 Determining the Direction of Rotation of a DC Motor	855
30-7 Speed Control	858
Section 12 - AC Machines	880
Unit 31 - Three-Phase Alternators	881
31-1 Three-Phase Alternators	882
31-2 The Rotor	886
31-3 The Brushless Exciter	886
31-4 Alternator Cooling	889
31-5 Frequency	890
31-6 Output Voltage	891
31-7 Paralleling Alternators	892
31-8 Sharing the Load	894
31-9 Field-Discharge Protection	895
Unit 32 - Three-Phase Motors	899
32-1 Three-Phase Motors	900
32-2 The Rotating Magnetic Field	901
32-3 Connecting Dual-Voltage Three-Phase Motors	911
32-4 Squirrel-Cage Induction Motors	917
32-5 Wound-Rotor Induction motors	934
32-6 Synchronous Motors	937
32-7 Selsyn Motors	944
Unit 33 - Single-Phase Motors	952
33-1 Single-Phase Motors	953

33-2 Split-Phase Motors	953
33-3 Resistance-Start Induction-Run Motors	957
33-4 Capacitor-Start Induction-Run Motors	965
33-5 Dual-Voltage Split-Phase Motors	967
33-6 Determining the Direction of Rotation for Split-Phase Motors ..	970
33-7 Capacitor-Start Capacitor-Run Motors	971
33-8 Shaded-Pole Induction Motors	974
33-9 Multispeed Motors	978
33-10 Repulsion-Type Motors	980
33-11 Construction of Repulsion Motors	980
33-12 Repulsion-Start Induction-Run Motors	983
33-13 Repulsion-Induction Motors	986
33-14 Single-Phase Synchronous Motors	987
33-15 Stepping Motors	989
33-16 Universal Motors	998

Appendix A

Trigonometric Functions - Natural Sines and Cosines	1006
---	------

Appendix B

Trigonometric Functions - Natural Tangents and Cotangents	1008
---	------

Appendix C

Identifying the Leads of Three-Phase, Wye-Connected, Dual-Voltage Motor	1010
--	------

Appendix D

Alternating Current Formulas	1014
------------------------------------	------

Appendix E

Greek Alphabet	1026
----------------------	------

Appendix F

Metals	1027
--------------	------

Appendix G	
Scientific Notation	1029
Appendix H	
Answers to Practice Problems	1034
Glossary	1050
Index	1067